

ASSIGNMENT – 1

DIGITAL SYSTEMS ES204

Guntas Singh Saran

guntassingh.saran@iitgn.ac.in

22110089

Nihar Shah

nihar.shah@iitgn.ac.in

22110237

PART – 1

SEL is a 3-bit input parameter with the following specifications:

SEL -> MULTIPLES OF

3'b000 -> 2

3'b001 -> 3

3'b010 -> 4

3'b011 -> 5

3'b100 -> 6

3'b101 -> 7

3'b110 -> 8

3'b111 -> 9

A is a 5-bit input parameter ranging from 5'b00000 till 5'b11111.

The module `multiple(A, SEL, OUT)` takes in **A** and **SEL** as input and produces a binary output **OUT** which is **1** if **A** is a multiple of **SEL** and **0** otherwise.

Thus, for a 5-bit number **A** and a given **SEL**, we have to map the 5 bits of **A** such that they correspond to one of the multiples of **SEL**.

This was achieved using K-Maps.

For Example:

- For **SEL** = 3'b000 (Multiples of 2 chosen) and **A** = $ABCDE$, the boolean logic would be:

$$\text{OUT} = \overline{E}.$$

- Similarly for **SEL** = 3'b011 (Multiples of 5 chosen) and **A** = $ABCDE$, the boolean logic would be:

$$\text{OUT} = (\overline{A}\overline{B}\overline{C}\overline{D}E) + (\overline{A}\overline{B}\overline{C}D\overline{E}) + (\overline{A}BCDE) + (\overline{A}\overline{B}C\overline{D}\overline{E}) + (A\overline{B}\overline{C}\overline{D}E) + (ABCD\overline{E})$$

Each of these six terms correspond to choosing **either** of the six multiples of 5 within 5-bit range:

```
5'b00101 -> 5
5'b01010 -> 10
5'b01111 -> 15
5'b10100 -> 20
5'b11001 -> 25
5'b11110 -> 30
```

VERILOG CODE

```
module multiple(A, SEL, OUT);

input [4:0] A;
input [2:0] SEL;
output reg OUT;

always @(*) begin
    case(SEL)

        0 : OUT = (~A[0]);

        1 : OUT = (~A[4] & ~A[3] & ~A[2] & A[1] & A[0]) |
                  (~A[4] & ~A[3] & A[2] & A[1] & ~A[0]) |
                  (~A[4] & A[3] & ~A[2] & ~A[1] & A[0]) |
                  (~A[4] & A[3] & A[2] & ~A[1] & ~A[0]) |
                  (~A[4] & A[3] & A[2] & A[1] & A[0]) |
                  (A[4] & ~A[3] & ~A[2] & A[1] & ~A[0]) |
                  (A[4] & ~A[3] & A[2] & ~A[1] & A[0]) |
                  (A[4] & A[3] & ~A[2] & ~A[1] & ~A[0]) |
                  (A[4] & A[3] & ~A[2] & A[1] & A[0]) |
                  (A[4] & A[3] & A[2] & A[1] & ~A[0]);

        2 : OUT = (~A[0] & ~A[1]);

        3 : OUT = (~A[4] & ~A[3] & A[2] & ~A[1] & A[0]) |
                  (~A[4] & A[3] & ~A[2] & A[1] & ~A[0]) |
                  (~A[4] & A[3] & A[2] & A[1] & A[0]) |
                  (A[4] & ~A[3] & A[2] & ~A[1] & ~A[0]) |
                  (A[4] & A[3] & ~A[2] & ~A[1] & A[0]) |
                  (A[4] & A[3] & A[2] & A[1] & ~A[0]);

        4 : OUT = (~A[4] & ~A[3] & A[2] & A[1] & ~A[0]) |
                  (~A[4] & A[3] & A[2] & ~A[1] & ~A[0]) |
                  (A[4] & ~A[3] & ~A[2] & A[1] & ~A[0]) |
                  (A[4] & A[3] & ~A[2] & ~A[1] & ~A[0]) |
                  (A[4] & A[3] & A[2] & A[1] & ~A[0]);

        5 : OUT = (~A[4] & ~A[3] & A[2] & A[1] & A[0]) |
                  (~A[4] & A[3] & A[2] & A[1] & ~A[0]) |
                  (A[4] & ~A[3] & A[2] & ~A[1] & A[0]) |
                  (A[4] & A[3] & A[2] & ~A[1] & ~A[0]);

    endcase
end
```

```
6 : OUT = (~A[0] & ~A[1] & ~A[2]);
```

```
7 : OUT = (~A[4] & A[3] & ~A[2] & ~A[1] & A[0]) |  
          (A[4] & ~A[3] & ~A[2] & A[1] & ~A[0]) |  
          (A[4] & A[3] & ~A[2] & A[1] & A[0]);
```

```
    endcase  
end
```

```
endmodule
```

TESTBENCH - 1

```
module testbench;

reg [4:0] A;
reg [2:0] SEL;
wire OUT;

mult1 bloop(.A(A), .SEL(SEL), .OUT(OUT));

initial begin
    $monitor($time, " A = %d, SEL = %d, OUT = %b", A, SEL, OUT);

    // SEL = 2, RANGE = 31
    SEL = 4'b000; A = 5'b00001; // <- 0
    #5 A = 5'b00010; // <- 1
    #5 A = 5'b00011; // <- 0
    #5 A = 5'b00100; // <- 1
    #5 A = 5'b00101; // <- 0
    #5 A = 5'b00110; // <- 1
    #5 A = 5'b00111; // <- 0
    #5 A = 5'b01000; // <- 1
    #5 A = 5'b01001; // <- 0
    #5 A = 5'b01010; // <- 1
    #5 A = 5'b01011; // <- 0
    #5 A = 5'b01100; // <- 1
    #5 A = 5'b01101; // <- 0
    #5 A = 5'b01110; // <- 1
    #5 A = 5'b01111; // <- 0
    #5 A = 5'b10000; // <- 1
    #5 A = 5'b10001; // <- 0
    #5 A = 5'b10010; // <- 1
    #5 A = 5'b10011; // <- 0
    #5 A = 5'b10100; // <- 1
    #5 A = 5'b10101; // <- 0
    #5 A = 5'b10110; // <- 1
    #5 A = 5'b10111; // <- 0
    #5 A = 5'b11000; // <- 1
    #5 A = 5'b11001; // <- 0
```

```

#5 A = 5'b11010; // <- 1
#5 A = 5'b11011; // <- 0
#5 A = 5'b11100; // <- 1
#5 A = 5'b11101; // <- 0
#5 A = 5'b11110; // <- 1
#5 A = 5'b11111; // <- 0


#5 $finish;
end

endmodule

```

RESULT – 1

 The waveform shows all multiples of 2 within the range 31



Notice the high output for every **2nd** interval for **15 HIGHS**.

(corresponding to **2, 4, 6, 8, 10, 12, 14, 16, 18, 20, 22, 24, 26, 28, 30**)

TESTBENCH - 2

```
module testbench;

reg [4:0] A;
reg [2:0] SEL;
wire OUT;

mult1 bloop(.A(A), .SEL(SEL), .OUT(OUT));

initial begin
    $monitor($time, " A = %d, SEL = %d, OUT = %b", A, SEL, OUT);


    // SEL = 6, RANGE = 20
    SEL = 4'b100; A = 5'b00001; // <- 0
    #5 A = 5'b00010; // <- 1
    #5 A = 5'b00011; // <- 0
    #5 A = 5'b00100; // <- 1
    #5 A = 5'b00101; // <- 0
    #5 A = 5'b00110; // <- 1
    #5 A = 5'b00111; // <- 0
    #5 A = 5'b01000; // <- 0
    #5 A = 5'b01001; // <- 0
    #5 A = 5'b01010; // <- 0
    #5 A = 5'b01011; // <- 0
    #5 A = 5'b01100; // <- 1
    #5 A = 5'b01101; // <- 0
    #5 A = 5'b01110; // <- 0
    #5 A = 5'b01111; // <- 0
    #5 A = 5'b10000; // <- 0
    #5 A = 5'b10001; // <- 0
    #5 A = 5'b10010; // <- 1
    #5 A = 5'b10011; // <- 0
    #5 A = 5'b10100; // <- 0

    #5 $finish;
end

endmodule
```

RESULT - 2

 The waveform shows all multiples of 6 within the range 20



Notice the high output for every **6th** interval for **3 HIGHS**.
(corresponding to **6, 12, 18**)

PART – 2

The 5x32 Decoder

The 5x32 decoder takes in 5 inputs and produces 32 outputs. For each 5-bit input, the decoder gives the **minterm** corresponding to that number.

For example, for $A = 25$ or `5'b11001`, the decoder will light up for the 25th output as this output corresponds to the **minterm** $AB\overline{C}\overline{D}E$.

Therefore, rather than defining the boolean logic for each 5-bit number as done in **PART – 1**, we just select the output index of the 5x32 decoder that corresponds to the 5-bit number.

We just need to add the corresponding multiples of **SEL** to an **OR** gate.

For example, for multiples of 7, we need to do

OUT = decoder[7] OR decoder[14] OR decoder[21] OR decoder[28].

We have created a separate module for the decoder within the same Verilog file and have instantiated its instance in the multiple module.

VERILOG CODE

[illegible]

```
endmodule
```

```
module multiple(A, SEL, OUT);
```

```
input [4:0] A;
```

```
input [2:0] SEL;
```

```
output reg OUT;
```

```
wire [31:0] decode;
```

```
decoder dec(.a(A), .out(decode));
```

```
always @(*) begin
```

```
    case(SEL)
```

```
        0 : OUT = decode[2] |  
            decode[4] |  
            decode[6] |  
            decode[8] |  
            decode[10] |  
            decode[12] |  
            decode[14] |  
            decode[16] |  
            decode[18] |  
            decode[20] |  
            decode[22] |  
            decode[24] |  
            decode[26] |  
            decode[28] |  
            decode[30];
```

```
        1 : OUT = decode[3] |  
            decode[6] |  
            decode[9] |  
            decode[12] |  
            decode[15] |  
            decode[18] |  
            decode[21] |  
            decode[24] |  
            decode[27] |  
            decode[30];
```

```

2 : OUT = decode[4] |
        decode[8] |
        decode[12] |
        decode[16] |
        decode[20] |
        decode[24] |
        decode[28];

3 : OUT = decode[5] |
        decode[10] |
        decode[15] |
        decode[20] |
        decode[25] |
        decode[30];

4 : OUT = decode[6] |
        decode[12] |
        decode[18] |
        decode[24] |
        decode[30];

5 : OUT = decode[7] | decode[14] | decode[21] | decode[28];

6 : OUT = decode[8] | decode[16] | decode[26];

7 : OUT = decode[9] | decode[18] | decode[27];

    endcase
end

endmodule

```

TESTBENCH - 1

```
module testbench;

reg [4:0] A;
reg [2:0] SEL;
wire OUT;

mult2 bloop(.A(A), .SEL(SEL), .OUT(OUT));

initial begin
    $monitor($time, " A = %d, SEL = %d, OUT = %b", A, SEL, OUT);

    // SEL = 5, RANGE = 31
    SEL = 4'b011; A = 5'b00001; // <- 0
    #5 A = 5'b00010; // <- 0
    #5 A = 5'b00011; // <- 0
    #5 A = 5'b00100; // <- 0
    #5 A = 5'b00101; // <- 1
    #5 A = 5'b00110; // <- 0
    #5 A = 5'b00111; // <- 0
    #5 A = 5'b01000; // <- 0
    #5 A = 5'b01001; // <- 0
    #5 A = 5'b01010; // <- 1
    #5 A = 5'b01011; // <- 0
    #5 A = 5'b01100; // <- 0
    #5 A = 5'b01101; // <- 0
    #5 A = 5'b01110; // <- 0
    #5 A = 5'b01111; // <- 1
    #5 A = 5'b10000; // <- 0
    #5 A = 5'b10001; // <- 0
    #5 A = 5'b10010; // <- 0
    #5 A = 5'b10011; // <- 0
    #5 A = 5'b10100; // <- 1
    #5 A = 5'b10101; // <- 0
    #5 A = 5'b10110; // <- 0
    #5 A = 5'b10111; // <- 0
    #5 A = 5'b11000; // <- 0
```

```

#5 A = 5'b11001; // <- 1
#5 A = 5'b11010; // <- 0
#5 A = 5'b11011; // <- 0
#5 A = 5'b11100; // <- 0
#5 A = 5'b11101; // <- 0
#5 A = 5'b11110; // <- 1
#5 A = 5'b11111; // <- 0


#5 $finish;
end

endmodule

```

RESULT – 1

 The waveform shows all multiples of 5 within the range 31



Notice the high output for every **5th** interval for **6 HIGHS**.
 (corresponding to **5, 10, 15, 20, 25, 30**)

TESTBENCH - 2

```
module testbench;

reg [4:0] A;
reg [2:0] SEL;
wire OUT;

mult2 bloop(.A(A), .SEL(SEL), .OUT(OUT));


initial begin
    $monitor($time, " A = %d, SEL = %d, OUT = %b", A, SEL, OUT);
    // SEL = 9, RANGE = 25
    SEL = 4'b111; A = 5'b00001; // <- 0
    #5 A = 5'b00010; // <- 0
    #5 A = 5'b00011; // <- 0
    #5 A = 5'b00100; // <- 0
    #5 A = 5'b00101; // <- 0
    #5 A = 5'b00110; // <- 0
    #5 A = 5'b00111; // <- 0
    #5 A = 5'b01000; // <- 0
    #5 A = 5'b01001; // <- 1
    #5 A = 5'b01010; // <- 0
    #5 A = 5'b01011; // <- 0
    #5 A = 5'b01100; // <- 0
    #5 A = 5'b01101; // <- 0
    #5 A = 5'b01110; // <- 0
    #5 A = 5'b01111; // <- 0
    #5 A = 5'b10000; // <- 0
    #5 A = 5'b10001; // <- 0
    #5 A = 5'b10010; // <- 1
    #5 A = 5'b10011; // <- 0
    #5 A = 5'b10100; // <- 0
    #5 A = 5'b10101; // <- 0
    #5 A = 5'b10110; // <- 0
    #5 A = 5'b10111; // <- 0
    #5 A = 5'b11000; // <- 0
    #5 A = 5'b11001; // <- 0
    #5 $finish;
end
```

```
end
```

```
endmodule
```

RESULT - 2

 The waveform shows all multiples of 9 within the range 25.



Notice the high output for every **9th** interval for **2 HIGHS**.

(corresponding to **9, 18**)