

ASSIGNMENT – 2

DIGITAL SYSTEMS ES204

Guntas Singh Saran

guntassingh.saran@iitgn.ac.in

22110089

Nihar Shah

nihar.shah@iitgn.ac.in

22110237

PART – 1

8-bit combined Adder-Subtractor using only **Full Adders**

The module has two 8-bit inputs (**A, B**). It has a **mode** input to select between Add/Sub

It has one 8-bit output **C** and **carry_borrow_out**

VERILOG CODE

```
module FullAdder(input [2:0] A, output SUM, output carry);
// A[2] = A, A[1] = B, A[0] = C_in
xor (SUM, A[0], A[1], A[2]);
and (a1, A[2], A[1]);
and (a2, A[1], A[0]);
and (a3, A[0], A[2]);
or (carry, a1, a2, a3);
endmodule

`timescale 1ns / 1ps

module Adder_sub8bit(
    input [7:0] A,
    input [7:0] B,
    input mode,
    output [7:0] SUM,
    output [7:0] gray,
    output carry
);
wire s1, s2, s3, s4, s5, s6, s7, s8, c1, c2, c3, c4, c5, c6, c7, c8;
wire S1, S2, S3, S4, S5, S6, S7, S8, C1, C2, C3, C4, C5, C6, C7, C8;
reg [7:0] SUM1;
reg carry1;
wire [7:0] gray0;

FullAdder add1(.A({A[0], B[0] ^ mode, mode}), .SUM(s1), .carry(c1));
FullAdder add2(.A({A[1], B[1] ^ mode, c1}), .SUM(s2), .carry(c2));
FullAdder add3(.A({A[2], B[2] ^ mode, c2}), .SUM(s3), .carry(c3));
FullAdder add4(.A({A[3], B[3] ^ mode, c3}), .SUM(s4), .carry(c4));
FullAdder add5(.A({A[4], B[4] ^ mode, c4}), .SUM(s5), .carry(c5));
FullAdder add6(.A({A[5], B[5] ^ mode, c5}), .SUM(s6), .carry(c6));
FullAdder add7(.A({A[6], B[6] ^ mode, c6}), .SUM(s7), .carry(c7));
FullAdder add8(.A({A[7], B[7] ^ mode, c7}), .SUM(s8), .carry(c8));

FullAdder add9(.A({~s1, 1'b0 , 1'b1}), .SUM(S1), .carry(C1));
```

```

FullAdder add10(.A({~s2, 1'b0, C1}), .SUM(S2), .carry(C2));
FullAdder add11(.A({~s3, 1'b0, C2}), .SUM(S3), .carry(C3));
FullAdder add12(.A({~s4, 1'b0, C3}), .SUM(S4), .carry(C4));
FullAdder add13(.A({~s5, 1'b0, C4}), .SUM(S5), .carry(C5));
FullAdder add14(.A({~s6, 1'b0, C5}), .SUM(S6), .carry(C6));
FullAdder add15(.A({~s7, 1'b0, C6}), .SUM(S7), .carry(C7));
FullAdder add16(.A({~s8, 1'b0, C7}), .SUM(S8), .carry(C8));

```

```

always @* begin
    if (mode == 1 & c8 == 0) begin
        SUM1 = {S8, S7, S6, S5, S4, S3, S2, S1};
        carry1 = C8;
    end
    else begin
        SUM1 = {s8, s7, s6, s5, s4, s3, s2, s1};
        carry1 = c8;
    end
end

```

```

assign SUM = SUM1;
assign carry = carry1;

```

```

GrayConverter gray1(.binary(SUM), .gray(gray0));
assign gray = gray0;
endmodule

```

```

module GrayConverter(input [7:0] binary, output [7:0] gray);
    assign gray[7] = binary[7] ;
    assign gray[6] = binary[6] ^ binary[7];
    assign gray[5] = binary[5] ^ binary[6];
    assign gray[4] = binary[4] ^ binary[5];
    assign gray[3] = binary[3] ^ binary[4];
    assign gray[2] = binary[2] ^ binary[3];
    assign gray[1] = binary[1] ^ binary[2];
    assign gray[0] = binary[0] ^ binary[1];
endmodule

```

TESTBENCH

```
module AdderTest4();

reg [7:0] A, B;
wire [7:0] SUM;
wire carry;
reg mode;

wire [7:0] gray;


Adder_sub8bit adder1(.A(A), .B(B), .mode(mode),
.SUM(SUM),.gray(gray), .carry(carry));

initial begin
    // mode = 1 -> Subtract
    // mode = 0 -> Add
    A = 8'b10001010; B = 8'b10100001; mode = 1'b0; // A = 138, B = 161
    #5 A = 8'b10010001; B = 8'b01010110; mode = 1'b1; // A = 145, B = 86
    #5 A = 8'b01010110; B = 8'b10010001; mode = 1'b1; // A = 86, B = 145
    #5 A = 8'b00001011; B = 8'b00101101; mode = 1'b0; // A = 11, B = 45
    #5 A = 8'b00001010; B = 8'b00010110; mode = 1'b1; // A = 10, B = 22
    #5 A = 8'b00010110; B = 8'b00001010; mode = 1'b1; // A = 22, B = 10
end


endmodule
```

RESULTS OF SIMULATION

 1. mode = 0, A = 00001011 (11), B = 00101101 (45)




 2. mode = 1, A = 00001010 (10), B = 00010110 (22)



GRAY CODE TESTING

 3. mode = 1, A = 01010110 (86), B = 10010001 (145)



4. mode = 1, A = 00001010 (10), B = 00010110 (22)

